

A+B

BEE-C202
SEMESTER EXAMINATION- MAY 2024
CLASS: B.TECH SEMESTER: II
BASIC ELECTRICAL ENGINEERING

Time: 3 hours

Max. Marks: 70

Note: Question Paper is divided into two sections: A and B. Attempt both the sections as per given instructions.

CO

BL

SECTION-A (SHORT ANSWER TYPE QUESTIONS)

Instructions: Answer any *five* questions in about 150 words each. Each question carries six marks.
(5 X 6 = 30 Marks)

Q-1 Determine the current in $5\ \Omega$ resistor (Fig.1) using mesh analysis (Matrix method)

Evaluation
 L1 &
 Analysis L3

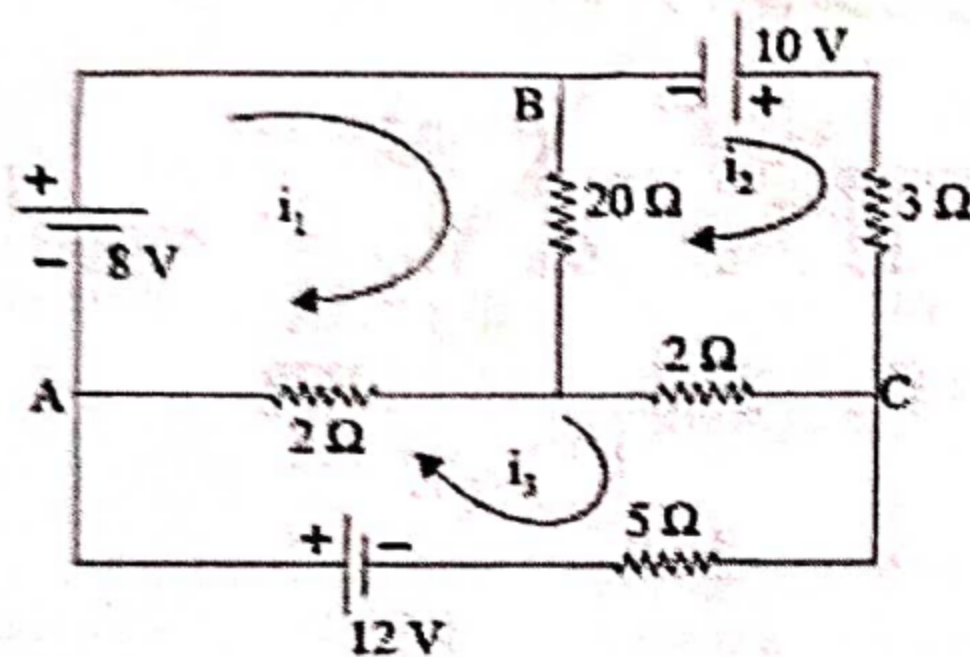


Fig.1

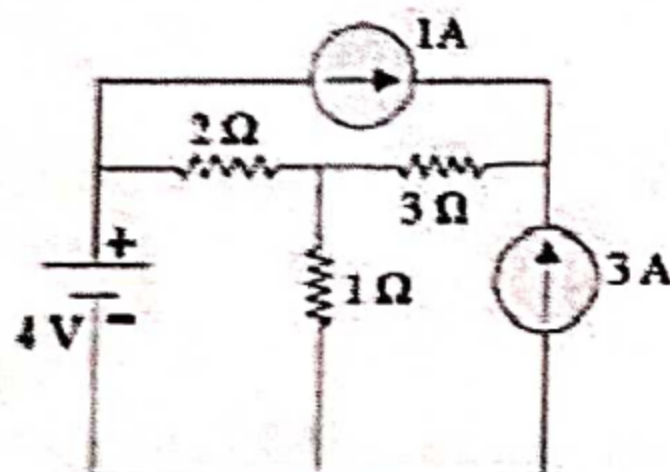


Fig.2

- | | | |
|--|-------|----------------------------------|
| Q-2 Find the current in $1\text{-}\Omega$ resistor using Thevenin's Theorem (Fig.2) | 4 | Evaluation L1 &
Analysis L3 |
| Q-3 Derive the expression for resonance frequency in R-L-C series circuit. | 2 | Analysis L3 |
| Q-4 Derive the expression for relation between Line voltage- Phase voltage Line current and Phase current in star connection | 2 | Analysis L3 |
| Q-5 Give the comparison between magnetic circuit and electrical circuit | 3 | Comparison L5 |
| Q-6 Explain the working principle of transformer | 2 | Knowledge L6 |
| Q-7 Explain Open Circuit (O.C) test of the transformer | 1 & 2 | Application L4 &
Knowledge L6 |

- | | | | |
|------|---|-------|---------------|
| Q-8 | Derive the E.M.F. equation of DC generator | 2 | Evaluation L1 |
| Q-9 | Describe the magnetization characteristics of D.C generator | 1 & 2 | Knowledge L6 |
| Q-10 | Describe the working principle of PMMC | 1 & 2 | Knowledge L6 |

SECTION-B (LONG ANSWER TYPE QUESTIONS)

CO BL

Instructions: Answer any *four* questions in detail. Each question carries 10 marks. (4 X 10 = Marks)

- | | | | |
|-----|--|-------|-------------------------------|
| Q-1 | State and prove the Maximum Power Transfer theorem | 1 & 2 | Application L4 & Knowledge L6 |
| Q-2 | A series resistance of $20\ \Omega$, an inductance of $0.2\ \text{H}$ and a capacitance of $100\ \mu\text{F}$ are connected in series across $220\ \text{V}$, $50\ \text{Hz}$ mains. Determine the following (i) Impedance (ii) Current voltage across R, L and C (iii) Power factor | 4 | Analysis L3 |
| Q-3 | Derive the expression for line voltage and phase volte in star connection | 2 | Evaluation L1 & Knowledge L6 |
| Q-4 | Explain the construction of transformer and derive the E.M.F equation of transformer. | 1 & 2 | |
| Q-5 | A 4-pole, wave wound armature has 720 conductors and is rotated at 1000 rev/min. If the useful flux is 20mwb , calculate the generated voltage. | 4 | Analysis L3 |
| Q-6 | Explain the working principle and slip torque characteristics of three-phase induction motor. | 1 & 2 | Knowledge L6 & Application L4 |
| Q-7 | Explain double revolving field theory to explain the working of induction motor | 1 & 2 | Knowledge L6 |
| Q-8 | Explain the measurement of three-phase power by two wattmeter methods. | 1 & 2 | Knowledge L6 |

14
62-8X6 62-8